

## Parallel Circuit Analysis Lesson Notes

### Learning Outcomes

- How are the variety of circuit parameters mathematically related for parallel circuits?
- How do you analyze a parallel circuit?

### Mathematical Equations

**Voltage Drops:** A charge making a loop of a parallel circuit will have a single voltage drop as it passes through one of the branches. Thus,

$$\Delta V_{\text{battery}} = \Delta V_1 = \Delta V_2 = \Delta V_3 = \dots$$

**Current:** The flow rate outside the branches and in the battery equals the sum of the branch currents:  $I_{\text{battery}} = I_1 + I_2 + I_3 + \dots$

The branch currents depend on the battery voltage and the resistance of the resistor in that branch:  $I_1 = \Delta V_{\text{battery}}/R_1$   $I_2 = \Delta V_{\text{battery}}/R_2$   $I_3 = \Delta V_{\text{battery}}/R_3$

**Equivalent Resistance:** The equivalent resistance ( $R_{\text{eq}}$ ) of a parallel circuit can be calculated using ...


$$1/R_{\text{eq}} = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

**For the three example problems, fill in all blanks. Show your work clearly.**
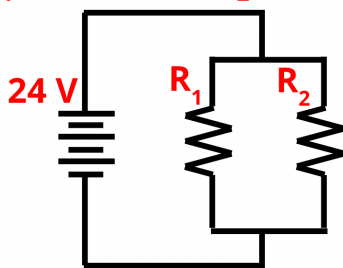
### Example Problem 1

Two resistors -  $4.0 \Omega$  and  $6.0 \Omega$  - are connected to a 24-volt power supply. Determine the equivalent resistance, the current in each resistor and battery, and the voltage drops across each resistor.

$$R_1 = 4.0 \Omega \quad R_2 = 6.0 \Omega$$



$$R_{\text{eq}} = \underline{\hspace{2cm}}$$

$$I_{\text{battery}} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \underline{\hspace{2cm}}$$


$$I_2 = \underline{\hspace{2cm}}$$

$$\Delta V_2 = \underline{\hspace{2cm}}$$
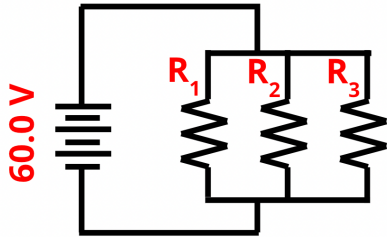
### Example Problem 2

Consider the 3-resistor circuit below. Determine all the blanks.

$$R_1 = 17\Omega \quad R_2 = 12\Omega \quad R_3 = 11\Omega$$



$$R_{\text{eq}} = \underline{\hspace{2cm}}$$

$$I_{\text{battery}} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$\Delta V_2 = \underline{\hspace{2cm}}$$


$$I_3 = \underline{\hspace{2cm}}$$

$$\Delta V_3 = \underline{\hspace{2cm}}$$
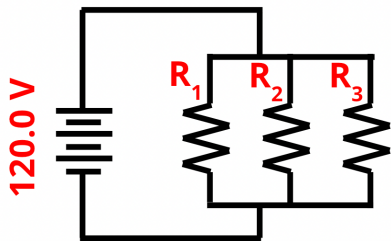
### Example Problem 3

Consider the 3-resistor circuit below. Determine all the blanks.

$$R_1 = 11\Omega \quad R_2 = 7.0\Omega \quad R_3 = 20.0\Omega$$



$$R_{\text{eq}} = \underline{\hspace{2cm}}$$

$$I_{\text{battery}} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$\Delta V_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$

$$\Delta V_3 = \underline{\hspace{2cm}}$$