

Series Circuit Analysis Lesson Notes

Learning Outcomes

- How are the variety of circuit parameters mathematically related for series circuits?
- How do you analyze a series circuit?

Mathematical Equations

Equivalent Resistance: the collection of resistors act together to create an overall total resistance ...

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$


Current: the current in a series circuit is everywhere the same - in every wire, resistor, and battery ...

$$I_{\text{battery}} = I_1 = I_2 = I_3 = \dots$$

Voltage Drops: The voltage drop (ΔV) across any resistor can be calculated using:

$$\Delta V_1 = I \cdot R_1 \qquad \Delta V_2 = I \cdot R_2 \qquad \Delta V_3 = I \cdot R_3$$

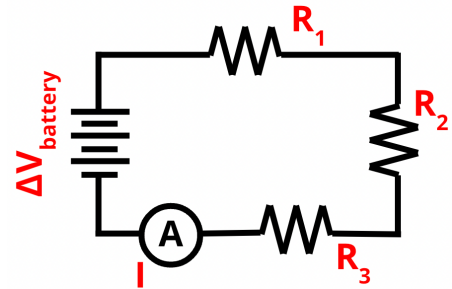As a check, use $\Delta V_{\text{battery}} = \Delta V_1 + \Delta V_2 + \Delta V_3$




Watch the video and record answers and solutions/notes for the following three Example Problems.

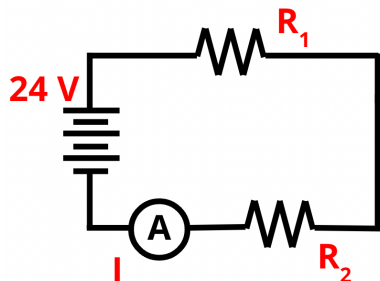Example Problem 1

Two resistors - 4.0Ω and 6.0Ω - are connected to a 24-volt power supply. Determine the equivalent resistance, the current in each resistor and battery, and the voltage drops across each resistor.

$$R_1 = 4.0 \Omega \qquad R_2 = 6.0 \Omega$$



$$R_{\text{eq}} = \underline{\hspace{4cm}} \qquad I_{\text{battery}} = \underline{\hspace{4cm}}$$


$$I_1 = \underline{\hspace{4cm}} \qquad \Delta V_1 = \underline{\hspace{4cm}}$$

$$I_2 = \underline{\hspace{4cm}} \qquad \Delta V_2 = \underline{\hspace{4cm}}$$

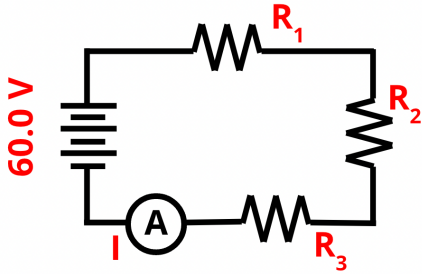Example Problem 2

Consider the 3-resistor circuit below. Determine all the blanks.

$$R_1 = 17\Omega \quad R_2 = 12\Omega \quad R_3 = 11\Omega$$



$$R_{eq} = \underline{\hspace{2cm}}$$

$$I_{battery} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$\Delta V_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$


$$\Delta V_3 = \underline{\hspace{2cm}}$$

Work Shown Here:

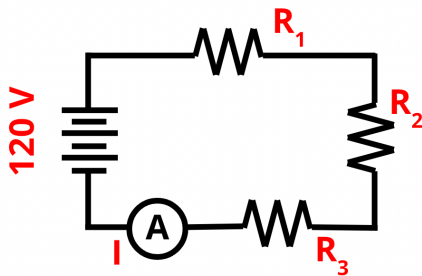Example Problem 3

Consider the 3-resistor circuit below. Determine all the blanks.

$$R_1 = 11\Omega \quad R_2 = 7\Omega \quad R_3 = 20\Omega$$



$$R_{eq} = \underline{\hspace{2cm}}$$

$$I_{battery} = \underline{\hspace{2cm}}$$

$$I_1 = \underline{\hspace{2cm}}$$

$$\Delta V_1 = \underline{\hspace{2cm}}$$

$$I_2 = \underline{\hspace{2cm}}$$

$$\Delta V_2 = \underline{\hspace{2cm}}$$

$$I_3 = \underline{\hspace{2cm}}$$

$$\Delta V_3 = \underline{\hspace{2cm}}$$

Work Shown Here: