


Series Circuit Relationships Lesson Notes

Learning Outcomes

- What are the important mathematical patterns and relationships associated with series circuits?
- How do you use these relationships?

Review:

Series Circuit

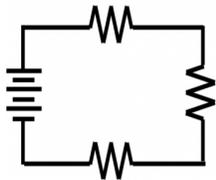

Only 1 pathway.
Every charge that makes the loop passes through every resistor.



As the number of resistors increases ...

- ... current decreases, and
- ... total resistance increases

Removing a bulb from its socket causes all the bulbs to be unlit.

Equivalent Circuits

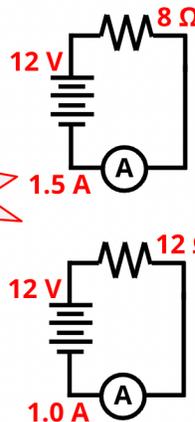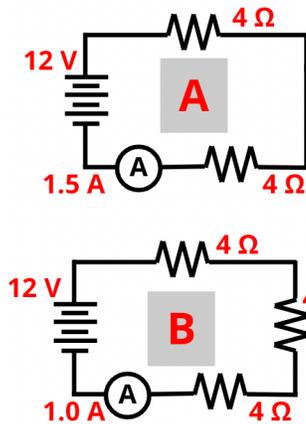In Circuit A, there are two 4-Ω resistors and a current of 1.5 A. In B, there are three resistors and a current of 1.0 A. As # of resistors ↑, the current ↓.




Having two 4-Ω resistors **is equivalent to** having one 8-Ω resistor. And having three 4-Ω resistors **is equivalent to** having a single 12-Ω resistor.

Equivalent Resistance

The **equivalent resistance** (R_{eq}) of a multiple-resistor circuit is the amount of resistance a single resistor must have to match the effect of the collection of resistors.

For series circuits:

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

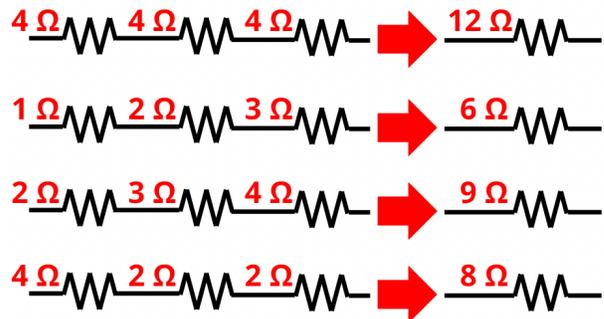


Current in Series Circuits

Current in a series circuit is everywhere the same.



$$I_{battery} = I_1 = I_2 = I_3$$

Current can be calculated using $\Delta V = I \cdot R$:

$$I = \Delta V_{battery} / R_{eq}$$

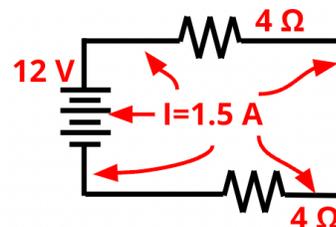

Practice

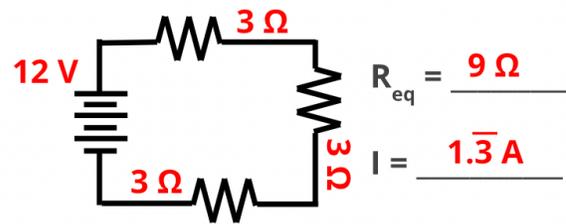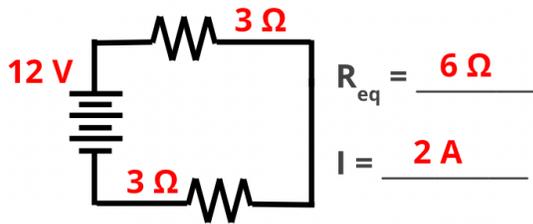


Electric Potential Difference

Every resistor causes a voltage drop or decrease in electric potential, represented by ΔV . The ΔV depends on the current and the resistance of the resistor.

$$\Delta V_1 = I \cdot R_1$$

$$\Delta V_2 = I \cdot R_2$$

$$\Delta V_3 = I \cdot R_3$$


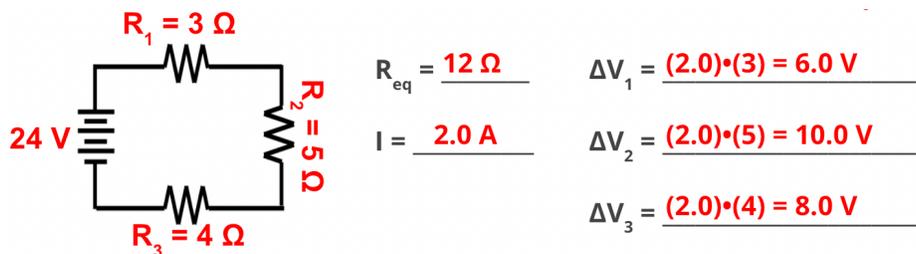


Note that the sum of all voltage drops (absolute value) is equal to the battery voltage.

$$\Delta V_{\text{battery}} = \Delta V_1 + \Delta V_2 + \Delta V_3 + \dots$$

Electric Potential Diagrams

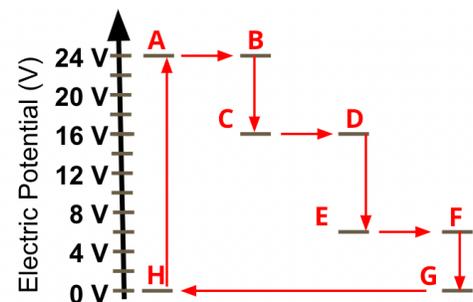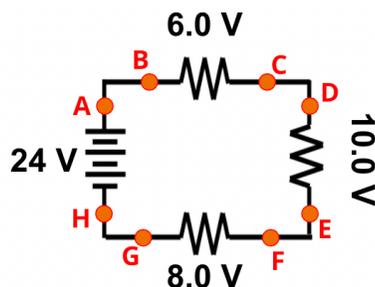Electric potential diagrams are conceptual tools that represent the relative electric potential for various locations on a circuit.




If charge gains 24 V

of potential in the battery, it will lose a total of 24 V as it passes through the external circuit.

Concept Practice

Three identical light bulbs are connected to a battery as shown. Which adjustments could be made to the circuit that would increase the current being measured at Z?

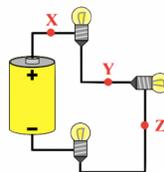- Increase the resistance of one of the bulbs.
- Increase the resistance of two of the bulbs.
- Decrease the resistance of two of the bulbs.
- Increase the voltage of the battery.
- Decrease the voltage of the battery.
- Remove one of the bulbs.



Three identical light bulbs are connected to a battery. Which one of the following statements about potential difference (ΔV) is **NOT** true? (Consider absolute value only.)

- The ΔV from A to C is greater than that from B to C.
- The ΔV from A to B is less than that from B to D.
- The ΔV from B to C is less than that from B to D.
- The ΔV from A to C is greater than that from B to D.
- The ΔV from A to D is the same as that across the battery.
- The ΔV from A to C is the same as that between B and D.

